

non trivial nullspace  $\Leftrightarrow \det = 0 \Leftrightarrow$  linearly dependent columns  $\Leftrightarrow$  non invertible

trivial nullspace  $\Leftrightarrow \det \neq 0 \Leftrightarrow$  linearly independent columns  $\Leftrightarrow$  invertible

Linearity:

Homogeneity  $f(ax) = a f(x)$

Superposition  $f(x_1 + x_2) = f(x_1) + f(x_2)$

If a row is, affine: does not fix the origin

000...10  $\Rightarrow$  infinite sols.

000...1n  $\Rightarrow$  no sols.

$n \in \mathbb{R}$   
but not 0

$$m \begin{bmatrix} \vdots \\ \vdots \\ \vdots \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = x_1 \begin{bmatrix} \vdots \\ \vdots \\ \vdots \end{bmatrix} + x_2 \begin{bmatrix} \vdots \\ \vdots \\ \vdots \end{bmatrix} + x_3 \begin{bmatrix} \vdots \\ \vdots \\ \vdots \end{bmatrix}$$

$$A\vec{x} = \vec{b} \Rightarrow A \in \mathbb{R}^{m \times n}, \vec{x} \in \mathbb{R}^n, \vec{b} \in \mathbb{R}^m$$

Conservative state transition matrix:  
columns all sum to 1

If  $\begin{bmatrix} A \\ B \\ C \end{bmatrix}$  represents state,

$$A = \begin{bmatrix} A \rightarrow A & B \rightarrow A & C \rightarrow A \\ A \rightarrow B & B \rightarrow B & C \rightarrow B \\ A \rightarrow C & B \rightarrow C & C \rightarrow C \end{bmatrix}$$

Vector Spaces:

- must contain  $\vec{0}$
- closed under vector addition
- closed under scalar multiplication

$\{\vec{v}_1, \vec{v}_2, \vec{v}_3, \dots, \vec{v}_n\}$  is the basis for  $\mathbb{V}$  vector space


if  $\vec{v}_1, \vec{v}_2, \dots, \vec{v}_n$  are lin. indep.

\* for any  $\vec{v} \in \mathbb{V}$ ,  $\vec{v}$  is a linear combination of  $\vec{v}_1, \vec{v}_2, \dots, \vec{v}_n$

dimension of  $\mathbb{V}$  = num. of basis vectors

$$A^T = a_{xy} \Rightarrow a_{yx}$$

Transresistance Amplifier

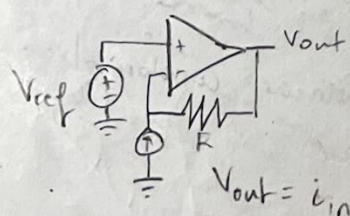

$$V_{out} = i_{in}(-R) + V_{ref}$$

Row Echelon Form:

- all nonzero rows are above all zero rows
- leading entries of a nonzero row are always to the right of the leading entries of the row above it
- all leading entries of non zero rows = 1

RREF:

- in REF
- each leading entry of a nonzero row is the only nonzero entry in its column

★ variables corresponding to columns containing leading entries are called basic variables, all others are called free variables

$$\text{span}(\vec{v}_1, \vec{v}_2, \dots, \vec{v}_n) = \left\{ \sum_{i=1}^n a_i \vec{v}_i \mid a_i \in \mathbb{R} \right\}$$

$$\text{span}(A) = \text{Col}(A) = \text{range}(A)$$

$\text{span}(\vec{v}_1, \vec{v}_2, \dots, \vec{v}_n) = \mathbb{R}^n$  if  $\vec{v}_1, \vec{v}_2, \dots, \vec{v}_n$  are linearly independent

$$A A^{-1} = A^{-1} A = I$$

$$[A \mid I] \rightarrow [I \mid A^{-1}]$$

using Gauss. Elim

if A is invertible, there exists a unique solution to  $A\vec{x} = \vec{b}$  for all  $\vec{b}$

Vector subspace  $U \subset V$  if it

- is closed under addition
- is closed under scalar multiplication
- contains  $\vec{0}$

Column Space =  $\text{span}(A)$

$\hookrightarrow \dim = \#$  of linearly indep. cols.

$$\dim(\text{span}(A)) \leq \min(m, n)$$

$$\text{rank}(A) = \dim(\text{span}(A))$$

$$\text{Null}(A) = \{ \vec{x} \mid A\vec{x} = \vec{0}, \vec{x} \in \mathbb{R}^n \}$$

$\hookrightarrow \vec{0}$  is trivial

Rank-Nullity Theorem:

$$m - \dim(\text{span}(A)) = \dim(\text{Null}(A))$$

$$m - \text{rank} = \dim(\text{Null}(A))$$



$\vec{v}$  is an eigenvector  
 $\vec{v} \neq \vec{0}$   
 $\vec{v}$  direction remains unchanged by  $A$   
 $A\vec{v} = \lambda\vec{v}$

$\lambda$  is an eigenvalue  
 $\hookrightarrow$  dictates scale factor of eigenvector

eigenvectors corresponding to distinct eigenvalues are lin. indep.

let  $\vec{x}$  be original vector  
 $\vec{x}'$  be transformed vector

$$\det \begin{bmatrix} a & b \\ c & d \end{bmatrix} = ad - bc$$

$$CBA\vec{x} = \vec{x}'$$

$\leftarrow$  order transformations are applied in

$\hookrightarrow$  factor by which area/volume changes as a result of transformation

$$\Rightarrow A\vec{v} - \lambda I\vec{v} = \vec{0}$$

$$(A - \lambda I)\vec{v} = \vec{0}$$

$$\det(A - \lambda I) = 0$$

Steady-state vector is eigenvector associated with  $\lambda = 1$

$$A \in \mathbb{R}^{m \times n}$$


$$B \in \mathbb{R}^{n \times p}$$

$$AB \in \mathbb{R}^{m \times p}$$

Counter clockwise

$$\begin{bmatrix} \cos \theta & -\sin \theta \\ \sin \theta & \cos \theta \end{bmatrix}$$

Resistive Touchscreen

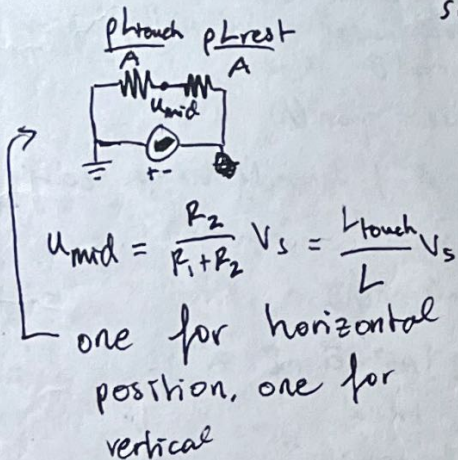

## Electrical Circuit Analysis






wire

resistor

open circuit

voltage source

current source

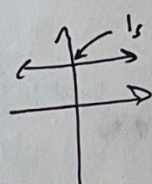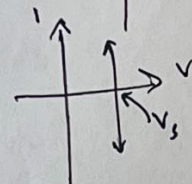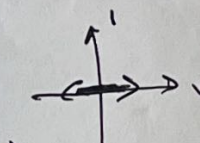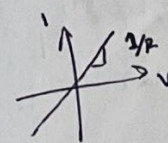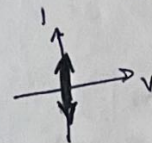


Ohm's Law  $V = IR$

Kirchoff's Law

Current:  $\sum_{\text{node}} i_k = 0$

Voltage:  $\sum_{\text{loop}} V_k = 0$

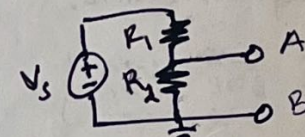



$$V_{AB} = V_s \left( \frac{R_2}{R_1 + R_2} \right)$$

$$I = \frac{dQ}{dt}$$

$$R = \frac{\rho L}{A}$$

$$P = IV = \frac{V^2}{R} = I^2 R$$

Dependent Sources:

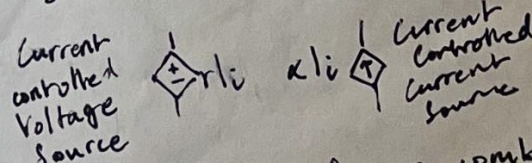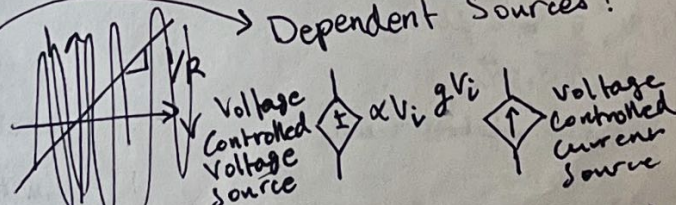

can describe as a linear combination of independent sources



# Superposition:


set all <sup>independent</sup> voltage sources to 0 (open wire)  $\leftarrow \infty$  resistance  
 set all current sources to 0 (open circuit)  $\leftarrow \infty$  resistance  
 calculate current/voltage of dependent element  
 add all values

Voltmeter:  $\infty$  resistance in parallel

Ammeter: 0 resistance in series

$$A \parallel B = \frac{AB}{A+B}$$

## Equivalence:

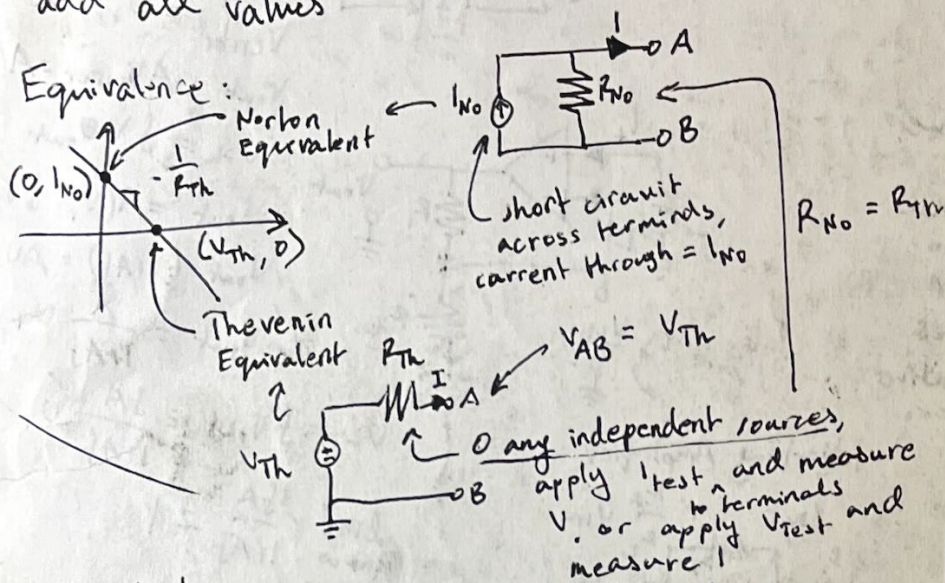


$$dE = V_c dq$$





$$dq = C dV_c$$

$$E = \frac{CV^2}{2} \leftarrow \text{voltage applied across capacitor}$$

$$V = \frac{I_s t}{C}$$

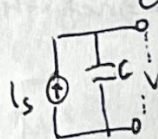

## Capacitive Touchscreen

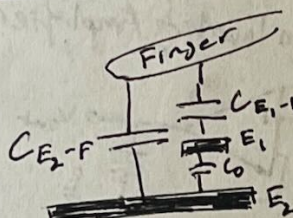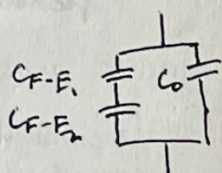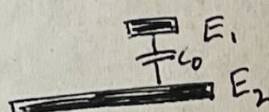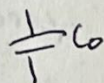

$$Q = CV_c$$

$$\Rightarrow \frac{dQ}{dt} = C \frac{dV_c}{dt} = I$$

$$\Rightarrow \int_0^t I dt = C \int_0^{V_c} dV_c$$

Assume  $I$  is constant over  $0-t$

$$\Rightarrow V_c(t) = \frac{I}{C} t + V_c(0)$$

$$C_{eq} = \frac{I_{test}}{\frac{dV_c}{dt}}$$


$$C_1 \parallel C_2 = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C} \Rightarrow C = \frac{C_1 C_2}{C_1 + C_2}$$

$$C = \frac{\epsilon A}{d} \leftarrow \text{area of overlap}$$


$$V_c(t) = \frac{I}{C} (t - t_0) + V_c(t_0)$$

## Op Amp




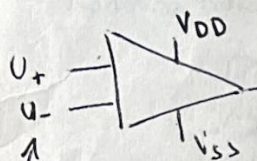


$$U_{out} = U_+ - U_-$$

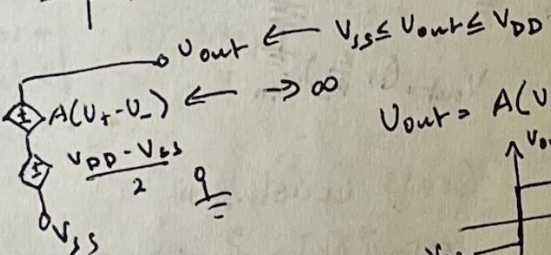$V_{ref}$  to use as comparator  
 $V_{DD}$  if  $U_+ > V_{ref}$   
 $V_{SS}$  if  $U_+ < V_{ref}$



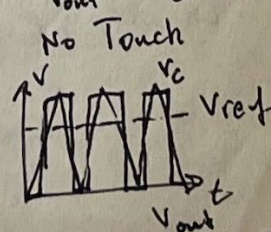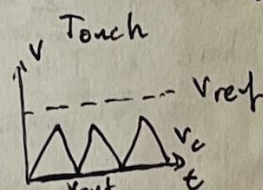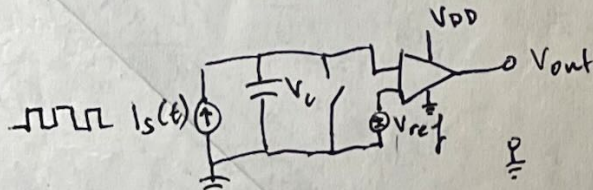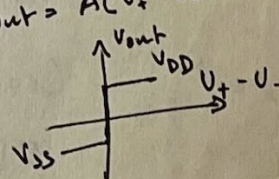
$$U_{out} = A(U_+ - U_-) + \frac{V_{DD} - V_{SS}}{2}$$




if no  $V_{out}$ , finger is present



# Negative Feedback

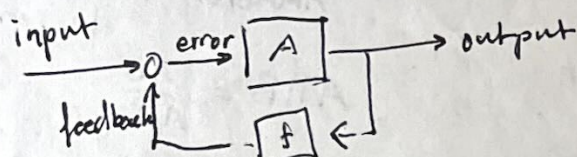

## Negative Feedback

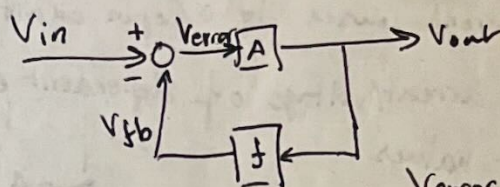


### Golden Rules:

$$I_- = I_+ = 0 \leftarrow \text{always true}$$

$$V_+ = V_- \leftarrow \text{error signal going into op amp} = 0$$

$A \rightarrow \infty$  implies only when negative feedback


### Unity Gain Buffer

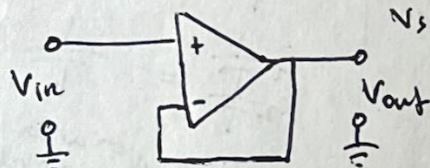


$$V_{in} = V_{out}$$

### Inverting Amplifier

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

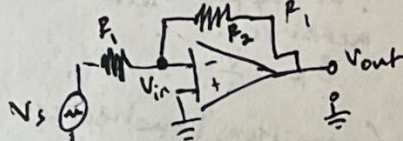

### Non Inverting Amplifier

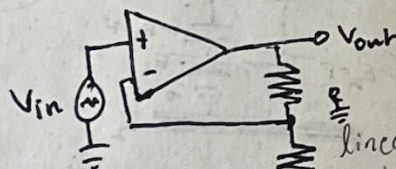

$$V_{out} = (1 + \frac{R_2}{R_1}) V_{in}$$

$$V_{error} = V_+ - V_-$$

$$V_{out} = A V_{error} = A(V_+ - V_-)$$

$$V_- = f V_{out}$$

$$V_{out} = A(V_+ - f V_{out})$$

$$V_{out} (1 + A f) = A V_+$$

$$V_{out} = \frac{A}{1 + A f} V_+$$

$$V_- = f V_{out} = \frac{f A}{1 + A f} V_+$$

$$\lim_{A \rightarrow \infty} \frac{f A}{1 + A f} = 1$$

$$\Rightarrow V_+ = V_-$$

### Test Negative feedback:

• zero out all independent sources

• "disk"  $V_{out}$ , if feedback is in opposite direction,  $\Rightarrow$  negative feedback

$$\text{Inner product } \langle \vec{x}, \vec{y} \rangle = \sum_{i=1}^n x_i y_i$$

$$= \vec{x}^T \vec{y}$$

linear, symmetric  $\rightarrow$  commutative

positive definite  $\rightarrow$  scalar multiplication

$\rightarrow$  distributive over vector addition

$\langle \vec{x}, \vec{y} \rangle = 0 \Rightarrow$  orthog

### Cross Correlation

$$\text{corr}_{\vec{x} \vec{y}}[k] = \sum_{i=-\infty}^{\infty} x[i] y[i-k]$$

where  $x[i], y[i] = 0$  for any  $i$   $\vec{x}, \vec{y}$  are not defined for

$$\hookrightarrow \text{corr}_{\vec{x} \vec{y}} \neq \text{corr}_{\vec{y} \vec{x}}$$

### Least Squares

$$A \vec{x} \approx \vec{b} \quad \|\vec{e}\| \perp \text{span}(A)$$

projection of  $\vec{b}$  onto  $\text{span}(A)$  minimizes  $\|\vec{e}\|$

$$\text{proj}_{\vec{a}_1} \vec{b} = \frac{\langle \vec{b}, \vec{a}_1 \rangle}{\langle \vec{a}_1, \vec{a}_1 \rangle} \vec{a}_1$$

$$\text{proj}_{\text{span}(A)} \vec{b} = \sum_{i=1}^k \frac{\langle \vec{b}, \vec{a}_i \rangle}{\langle \vec{a}_i, \vec{a}_i \rangle} \vec{a}_i$$

$$A^T (\vec{b} - A \vec{x}) = \vec{0} \Rightarrow A^T A \vec{x} = A^T \vec{b}$$

where  $\vec{a}_i$  is a column of  $A$

Net Power in closed circuit = 0

### Euclidian Norm

$$\sqrt{\langle \vec{x}, \vec{x} \rangle}$$

$$\|\vec{x}\| \geq 0$$

$$\|\vec{x}\| = 0 \text{ if } \vec{x} = \vec{0}$$

$$\|\alpha \vec{x}\| = |\alpha| \|\vec{x}\|$$

$$\|\vec{x} + \vec{y}\| \leq \|\vec{x}\| + \|\vec{y}\| \quad (\text{Triangle Inequality})$$

$$\langle \vec{x}, \vec{y} \rangle = \cos \alpha \text{ if } \alpha \text{ is angle between unit vectors } \vec{x} \text{ and } \vec{y}$$

$$|\langle \vec{x}, \vec{y} \rangle| \leq \|\vec{x}\| \|\vec{y}\|$$

(Cauchy-Schwartz Inequality)



$$\begin{bmatrix} 2(\vec{a}_1 - \vec{a}_2)^T \\ 2(\vec{a}_1 - \vec{a}_3)^T \end{bmatrix} \vec{x} = \begin{bmatrix} \|\vec{a}_1\|^2 - \|\vec{a}_2\|^2 - d_1^2 + d_2^2 \\ \|\vec{a}_1\|^2 - \|\vec{a}_3\|^2 - d_1^2 + d_3^2 \end{bmatrix}$$

$\vec{a}$  is coordinates of sender  
d is distance from sender to receiver

Left Nullspace

$$\{ \vec{x} : A^T \vec{x} = \vec{0} \}$$


Let  $M = \begin{bmatrix} a & b \\ c & d \end{bmatrix}$

$$\frac{1}{|M|} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$


If matrix has more columns than rows (more unknowns than eqs), a unique solution does not exist

Current Divider:

$$I_{R_1} = I_s \frac{R_2}{R_1 + R_2}$$

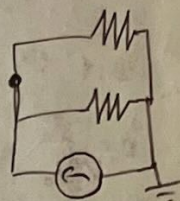


Non-Inverting Amplifier

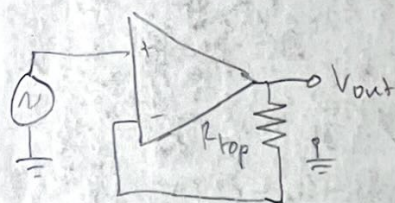

$$V_{out} = V_{in} \left( 1 + \frac{R_{top}}{R_{bottom}} \right) - V_{ref} \left( \frac{R_{top}}{R_{bottom}} \right)$$

$$\text{null}(A) = \text{null}(A^T A)$$

Voltage Summer

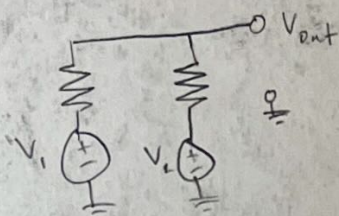


$$V_{out} = V_1 \left( \frac{R_2}{R_1 + R_2} \right) + V_2 \left( \frac{R_1}{R_1 + R_2} \right)$$


$$\langle \vec{v}, \vec{w} \rangle = \vec{v}^T Q \vec{w}$$

Q must be symmetric  
 $Q = Q^T$

Inverting Amplifier

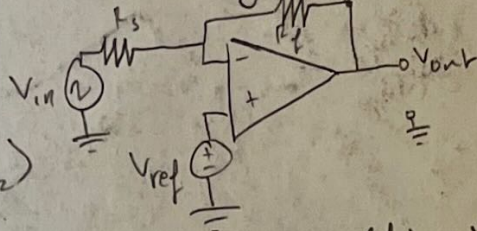
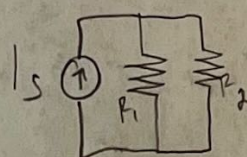
$$V_{out} = V_{in} \left( -\frac{R_f}{R_s} \right) + V_{ref} \left( \frac{R_f}{R_s} + 1 \right)$$



$$I_{R_1} = \frac{R_2}{R_1 + R_2} I_s$$

Current Divider